

Memo No.
Date / /



在: $V_A = 2V$
 $V_P = V_A = 2V$
 $V_{out} = 5V$




理想运放输入阻抗无穷大
当反馈被引入负反馈时 $V_A = V_P$

扫描文稿

PDF 文稿 · 572 KB

Memo No.
Date / /

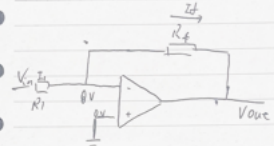

$$I_1 = \frac{V_{in} - 0}{R_1}$$
$$I_f = \frac{0V - V_{out}}{R_f}$$

$$\frac{V_{in} - 0}{R_1} = -\frac{V_{out}}{R_f}$$

$$V_{in} \cdot \left(-\frac{R_f}{R_1}\right) = V_{out}$$

反向放大器


扫描文稿

PDF 文稿 · 516 KB

Memo No.
Date / /

LM358

同相比例运算

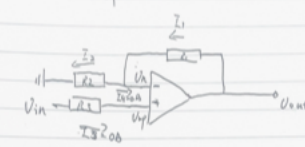

$$V_{R3} = R_3 \cdot I_3 = 0$$
$$V_P = V_{in} - V_{R3} = V_{in}$$
$$V_A = V_{out} - V_{R1}$$

$$V_A \approx V_P \approx V_{in}$$
$$I_2 = (V_A - 0) / R_2$$
$$I_1 = I_2$$
$$I_1 = (V_{out} - V_A) / R_1$$


$$V_{out} = \left(\frac{R_1}{R_2} + 1\right) V_{in}$$


扫描文稿

PDF 文稿 · 1.2 MB

Memo No.
Date / /

双电源正负电压

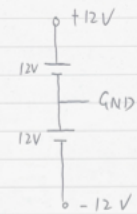

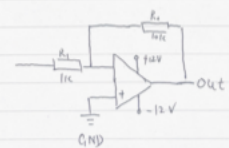

扫描文稿

PDF 文稿 · 680 KB

